

# Module 10A – Introduction to Circuitry

Justin Chen<sup>1</sup>, Anya Bekhtel<sup>1</sup>

<sup>1</sup>BMES Cell Team

April 2021

# Outline

1 Basic Circuit Elements

2 Kirchhoff's Laws

# Outline

1 Basic Circuit Elements

2 Kirchhoff's Laws

## Definition

A **resistor** is a linear, two-terminal circuit element whose function is to reduce current flow along a path.


- The symbol for a resistor is as follows:



- The characteristic equation for a resistor is defined by **Ohm's Law**

$$v \equiv iR \quad (1)$$


# Resistors in Series

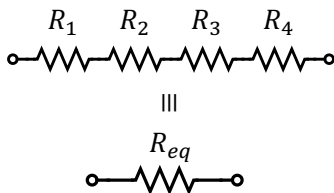

- We can define an equivalent resistor  $R_{eq}$  for a set of resistors in series by the following relationship:

$$R_{eq} = R_1 + R_2 + \dots + R_N = \sum_{i=1}^N R_i \quad (2)$$

# Resistors in Parallel

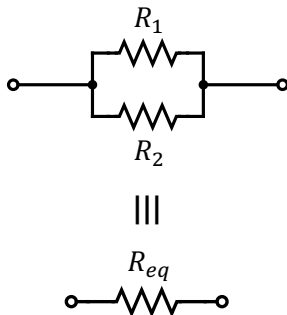

- We can define an equivalent resistor  $R_{eq}$  for a set of resistors in parallel by the following relationship:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} = \sum_{i=1}^N \frac{1}{R_i} \quad (3)$$

# Power Dissipated by a Resistor

- The power dissipated by a resistor is given by:

$$P = iv \quad (4)$$

- Combining equations (1) and (4) gives us two other ways to define power:


$$P = i^2 R = \frac{v^2}{R} \quad (5)$$

# Capacitors
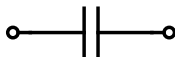
## Definition

A **capacitor** is a linear, two-terminal circuit element whose function is to store energy in an *electric* field  $\vec{E}$ .

- The symbol for a capacitor is as follows:



- The characteristic equation for a capacitor is defined as follows:

$$i \equiv C \frac{dv}{dt} \quad (6)$$



# Capacitors in Series and Parallel

- We can define an equivalent capacitor  $C_{eq}$  for a set of capacitors in series by the following relationship:

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_N} = \sum_{i=1}^N \frac{1}{C_i} \quad (7)$$

- We can define an equivalent capacitor  $C_{eq}$  for a set of capacitors in parallel by the following relationship:

$$C_{eq} = C_1 + C_2 + \dots + C_N = \sum_{i=1}^N C_i \quad (8)$$

## Definition

An **inductor** is a linear, two-terminal circuit element whose function is to store energy in a *magnetic* field  $\vec{B}$ .

- The symbol for a capacitor is as follows:



- The characteristic equation for an inductor is defined as follows:

$$v \equiv L \frac{di}{dt} \quad (9)$$

# Inductors in Series and Parallel

- We can define an equivalent inductor  $L_{eq}$  for a set of inductors in series by the following relationship:

$$L_{eq} = L_1 + L_2 + \dots + L_N = \sum_{i=1}^N L_i \quad (10)$$

- We can define an equivalent inductor  $L_{eq}$  for a set of inductors in parallel by the following relationship:

$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_N} = \sum_{i=1}^N \frac{1}{L_i} \quad (11)$$

# Principle of Duality

- In Physics, the *principle of duality* holds for a lot of concepts and quantities
- The constitutive equations between duals are opposites of one another
- For instance:
  - A parallel circuit is the dual of a series circuit
  - An inductor  $L$  is the dual of a capacitor  $C$

$$v_L = L \frac{di}{dt} \iff i_C = C \frac{dv_C}{dt}$$

$$L_{eq,series} = \sum_{i=1}^N L_i \iff C_{eq,series} = \sum_{i=1}^N \frac{1}{C_i}$$

$$L_{eq,parallel} = \sum_{i=1}^N \frac{1}{L_i} \iff C_{eq,parallel} = \sum_{i=1}^N C_i$$

# Steady State Analysis of DC Circuits

- Capacitors act as an open circuit at  $t \rightarrow \infty$ 
  - Will later show this in the derivation of  $v_c$  in an RC circuit
- Inductors act as a short circuit at  $t \rightarrow \infty$

# Outline

1 Basic Circuit Elements

2 Kirchhoff's Laws

- Kirchoff's Laws are used as the starting point for derivations of complex circuits
- After combining Kirchoff's Laws with the characteristic equations described in (1), (6), and (9), we end up with an ordinary differential equation
- This differential equation can be used to solve for voltage and current at certain points in the circuit

# Voltage and Current Sources

- Batteries are the source for voltage and current in a circuit
- Typically, only one quantity is given and not the other



Voltage Source



Current Source

- For a voltage source, the current travels through the circuit from the positive end to the negative end
- For a current source, the current travels in the direction of the arrow



# Kirchoff's Voltage Law


## Definition

**Kirchoff's Voltage Law** (KVL) states that the sum of all voltage drops around a loop is equal to zero.

$$\sum_{\text{loop}} v_j = 0$$
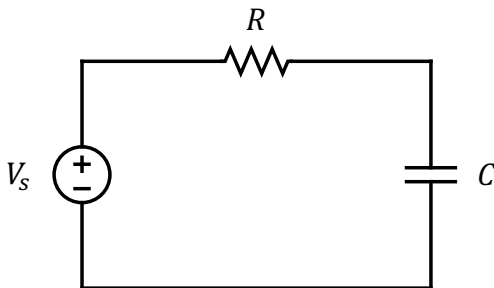
# KVL Example

- For the circuit below, write down the characteristic differential equation using Kirchoff's Voltage Law as a starting point.





# Kirchoff's Current Law


## Definition

**Kirchoff's Current Law** (KCL) states that the sum of all currents entering or leaving a node is equal to zero.

$$\sum_{\perp} i_j = 0$$
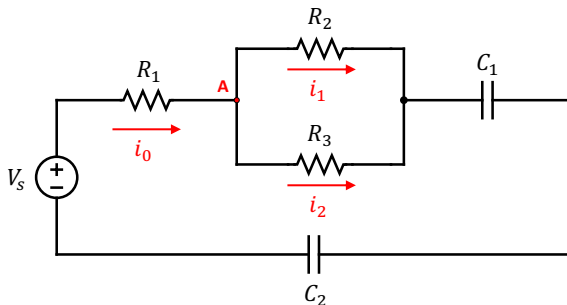
# KCL Example

- For the circuit below, write down the KCL equation for node A in terms of  $i_0$ ,  $i_1$ , and  $i_2$ .





# Applications of Kirchoff's Laws

We will derive the characteristic equations for the following circuits in the slides to come.

- 1st Order Circuits
  - RC Circuits
  - RL Circuits
- 2nd Order Circuits
  - RLC Circuits

